

# MHV FPGA Workshop

Series 1

# Welcome

- \* Stephen Davies, MHV login sjdavies
- \* Space facilities
  - \* Bathrooms/Refreshments
  - \* WiFi
- \* Free workshop, donations welcome



# Series Goals

- \* FPGA programming in Verilog
  - \* Assume no Verilog skills
  - \* Some programming experience e.g. Arduino
- \* Assume no digital design skills
- \* 8 bit processor as challenge


# Today's Goals

- \* Basic Verilog coding and testing
- \* AVR Architecture basics
- \* CPU outline
- \* Implement 3 basic instructions
- \* Parallel thinking


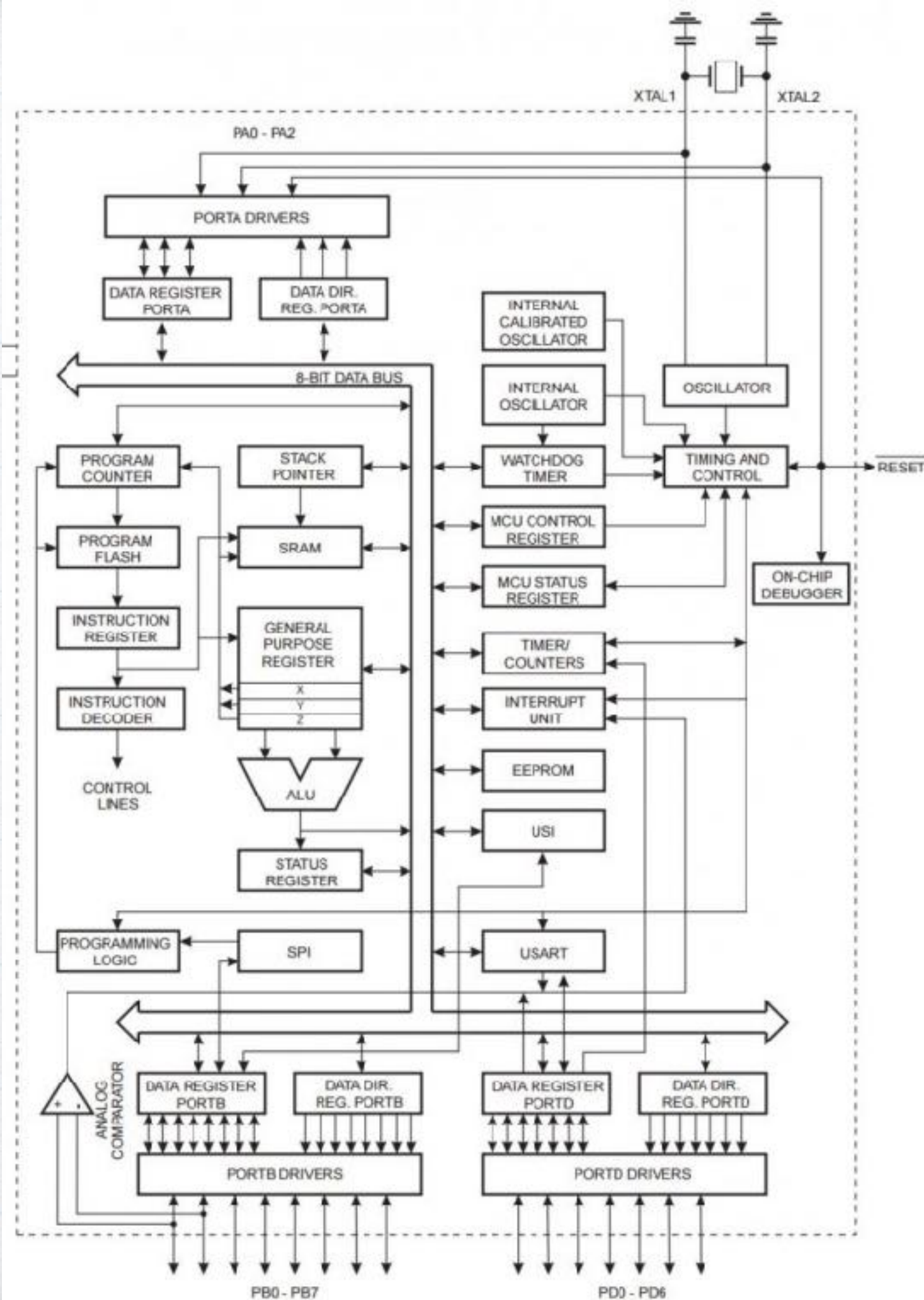
# Atmel AVR

- \* First released 1996
- \* Device family
  - \* 6 pins, attiny10, USD 0.24
  - \* 64 pins, atmega2561, USD 8.51
- \* Processor core very consistent over entire family
- \* Arduino uses atmega328







# AVR Architecture

- \* 8 bit
- \* Instructions are 16 bits wide
  - \* 2k flash = 1k instructions
- \* Register file
  - \* 32 x 8 bits (in general)
  - \* 16 x 8 bits (some tiny)

# Stage 1 Roadmap

 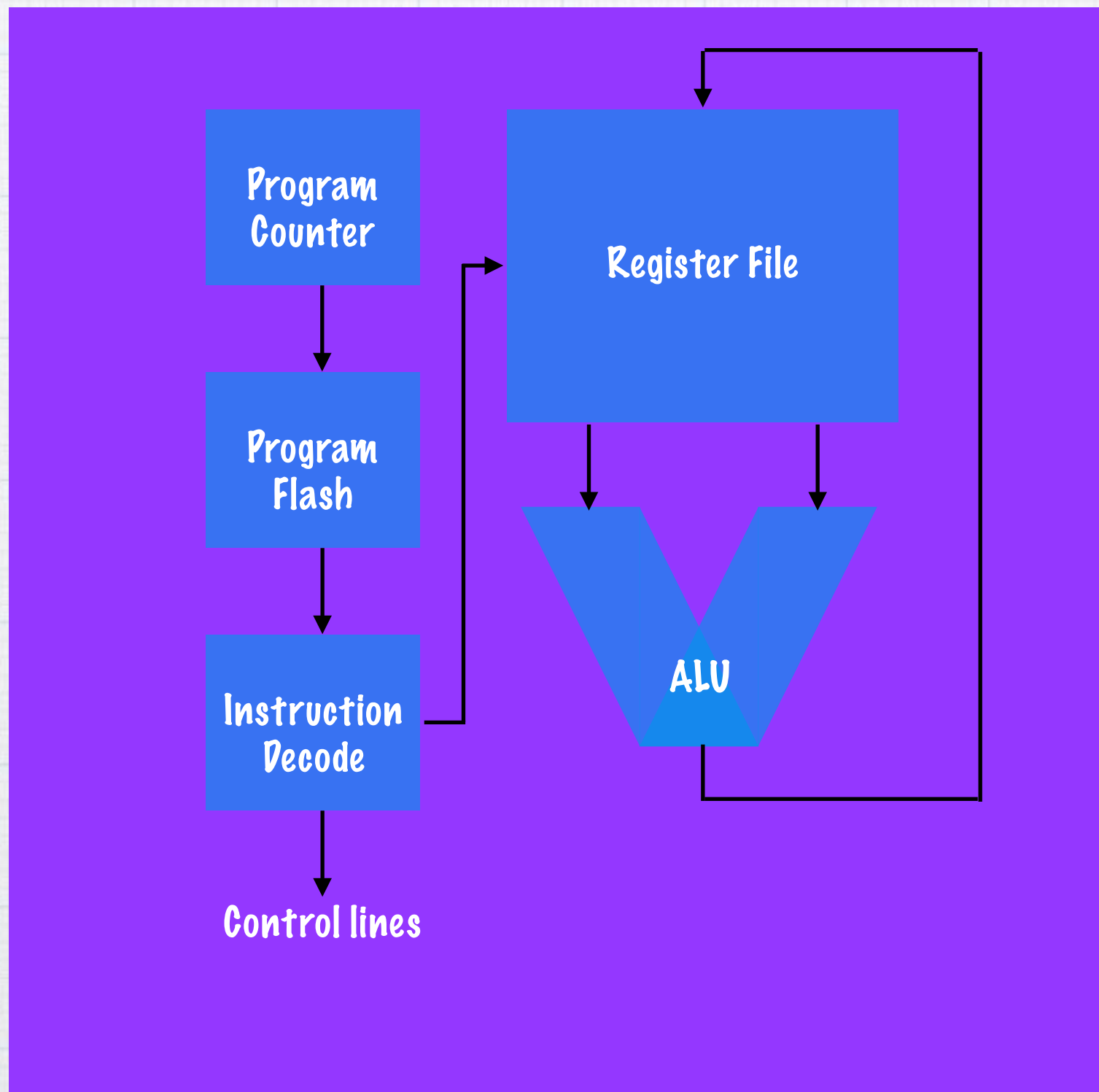

Tasty...



# Demo 1

- \* Workshop repository tour
- \* Design notes
- \* External resources
- \* Exercise structure
- \* Sample files

# Lab 02 - Project Setup

- \* Create Vivado project
- \* Copy template files
- \* Add files to project
- \* Run behavioural simulation
- \* Look around some of the .v files




# Combinational Logic

- \* Output value(s) are derived from current inputs
  - \* Has no 'state' (memory)
- \* Combination of basic functions
  - \* Not
  - \* And
  - \* Or
- \* ALU is purely combinational logic
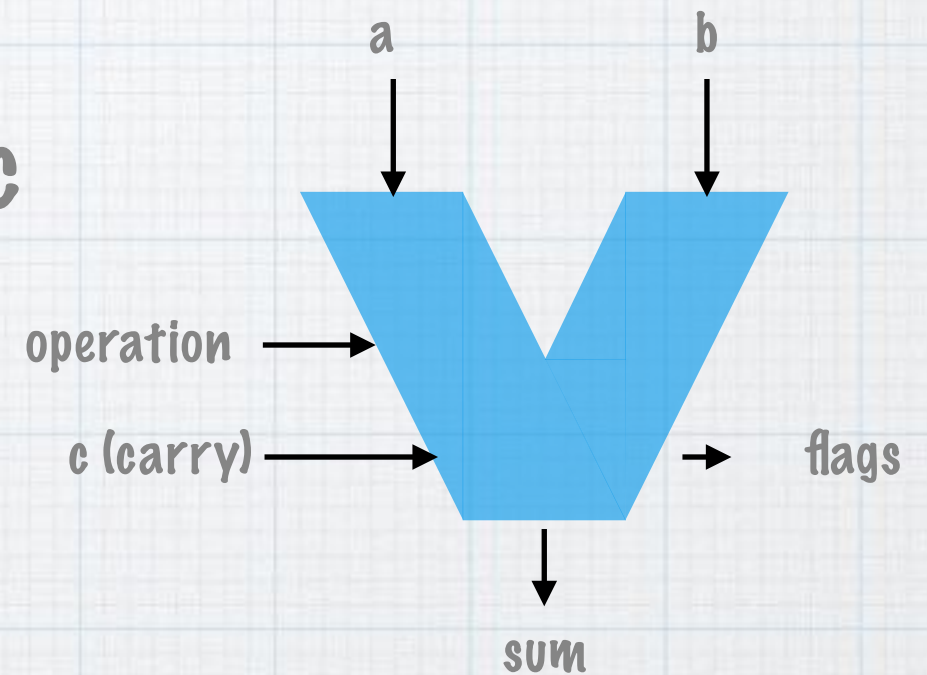
# ALU


- \* Arithmetic Logic Unit
- \* Output is function of a, b and c
  - \* +, -, AND, OR, XOR, SHIFT
- \* Flags - boolean conditions
  - \* C (carry)
  - \* Z (zero)





# Simplified ALU

fn	name	sum
2'b00	AND	a AND b
2'b01	OR	a OR b
2'b10	XOR	a XOR b
2'b11	PASSB	b

 



```

module logic (
    input      [1:0]    fn,
    input      [7:0]    a,
    input      [7:0]    b,
    output reg  [7:0]    sum,
    output      s, v, n, z


);

always @*
    case (fn)
        default: sum = 8'b0;
    endcase

// Flag logic, leave this bit alone
assign s = sum[7];
assign v = 1'b0;
assign n = sum[7];
assign z = ~| sum;

endmodule

```

 



# Verilog

- \* Verilog 2001 standard
- \* C like
- \* Case-sensitive
  - \* DON'T use case alone to separate signals
- \* Less verbose than VHDL
- \* Vivado has free Verilog Simulation & Synthesis

# Verilog Logic Values

- \* Four valued logic system - 0, 1, X and Z
- \* Subtle Simulation v Synthesis differences

Value	Simulation	Synthesis
0	0	0
1	1	1
X	undefined	n/a
Z	tri-state (out) Z = X (input)	tri-state (out)





# Basic Logic Equations

0	1
1	0
X	X

Not

	0	1	X
0	0	0	0
1	0	1	X
X	0	X	X

And

	0	1	X
0	0	1	X
1	1	1	1
X	X	1	X

Or


	0	1	X
0	0	1	X
1	1	0	X
X	X	X	X

Xor
 
# Module

- \* Describes 'components'
  - \* Basic gates - NOT, AND, OR
  - \* System components - Microblaze, DDR3 memory controller

```
module logic (  
    input      [1:0]    fn,  
    input      [7:0]    a,  
    input      [7:0]    b,  
    output reg  [7:0]    sum,  
    output      s, v, n, z  
);  
  
// module_items
```






# Instantiation

- \* 'Creates' a module instance
  - \* 'wires' a component into the circuit
  - \* Same as Object Oriented program

```
logic u1 (  
    .fn(funk),  
    .a(a), .b(b), .sum(out1),  
    .s(s), .v(v), .n(n), .z(z)  
);
```
 
```
logic u2 (  
    .fn(funky),  
    .a(a), .b(b), .sum(out2)  
);
```





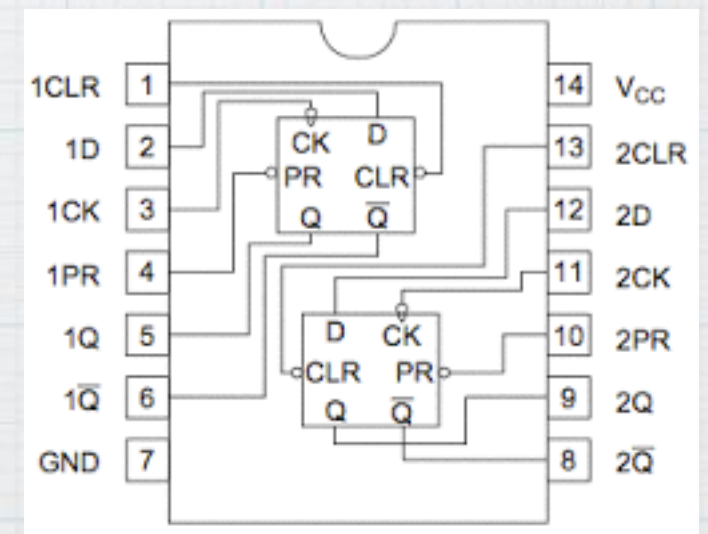
# Ports

- \* Define connections to a module
- \* Direction - input, output and inout
- \* Data type, range and name

```
module logic (  
    input      [1:0]    fn,  
    input      [7:0]    a,  
    input      [7:0]    b,  
    output reg  [7:0]    sum,  
    output      s, v, n, z  
);
```





# Data Type - Wire

- \* Network data type
  - \* Connects modules together
  - \* Has no 'state'
- \* The default type
- \* Multiple outputs can be wired together
  - \* Resolution function
- \* Used with **assign**

# Data Type - Reg

- \* Variable data type
- \* Holds state
- \* Used in procedural blocks
  - \* initial
  - \* always



# Scalars and Vectors

- \* Scalar - single bit
- \* Vector - multiple bits
  - \* Specified by range [ MSB : LSB ]
  - \* MSB (leftmost), LSB (rightmost)

```
wire      a;          // scalar
reg       b, c;
```

```
wire [7:0] x;          // vector
wire [15:8] y;
reg  [0:7] z;
```

```
      x[7]             // scalar or vector?
```



```

module logic(
    input      [1:0]    fn,
    input      [7:0]    a,
    input      [7:0]    b,
    output reg  [7:0]    sum,
    output      s, v, n, z


);

always @*
    case (fn)
        default: sum = 8'b0;
    endcase

// Flag logic, leave this bit alone
assign s = sum[7];
assign v = 1'b0;
assign n = sum[7];
assign z = ~| sum;

endmodule

```

 



# Literals

- \* Hardcoded constant values
  - \* `<value>` - unsigned decimal number (32)
  - \* `<size> ' <s> <base> <value>`
- \* Common bases - b/B, d/D, h/H

```
42;           // 32 bits, hex 0000002A
```

```
8'b00000000; // 8 bits, binary 00000000
```

```
4'D5;        // 4 bits, binary 0101
```

# Continuous Assignment

- \* **assign** keyword
- \* LHS data type must be wire
- \* RHS is expression of wire/reg

```
assign s = sum[7];  
assign v = 1'b0;  
assign n = sum[7];  
assign z = ~| sum;
```



# Procedures

- \* 'Wrappers' for procedural statements
  - \* =, case, if-then-else
- \* Two kinds
  - \* initial
  - \* always

# initial

- \* Starts at simulation time 0
- \* Enclosed statements execute once
- \* Testbenches

```
initial begin
    errors = 0;
    $display($time, " << Starting simulation >>");
    #10;

    for (test = 0; test < TESTS; test = test + 1) begin
```



# always

- \* Never ends
- \* Normally has a sensitivity list

```
always @( ) begin
```

```
...
```

```
end
```

```
// Combinational logic
```

```
@*           // Wildcard, use this!
```

```
@(a or b)    // Verilog 1995 style
```

```
@(a, b)      // Verilog 2001 style
```

```
// Sequential logic
```

```
@(posedge clk)
```



# case Statement

```
case ( expression )  
  case_item:           statement or statement_group  
  case_item, case_item: statement or statement_group  
  default:             statement or statement_group  
endcase
```

```
wire [7:0] a, [7:0] b;  
wire [1:0] fn;  
reg  [7:0] sum;  
...  
case (fn)  
  2'b01:    sum = a | b;  
  2'b10:    sum = a ^ b;  
  default:  sum = a & b;  
endcase
```



# Parallelism

- \* Procedures and continuous assignments operate in parallel

module  
logic

```
assign  
s = sum[7]
```

```
assign  
v = 1'b0
```

```
assign  
n = sum[7]
```

```
assign  
z = ~|sum
```

```
always @*  
case (fn)
```

# Bitwise Operators

**\*** Binary -  $\langle \text{value} \rangle$  OP  $\langle \text{value} \rangle$

```
a & b           // bitwise AND  
a | b           // bitwise OR  
a ^ b           // bitwise XOR
```



# Lab 03 - ALU Logic

- \* Use code template, extending CASE for

- \* AND

- \* OR

- \* XOR

- \* PASSB


- \* Run behavioural simulation

- \* Make all tests work

- \* Don't over think it, 4 lines is sufficient!

# ALU Logic Module


fn	name	sum
2'b00	AND	$a \& b$
2'b01	OR	$a   b$
2'b10	XOR	$a \wedge b$
2'b11	PASSB	b

 


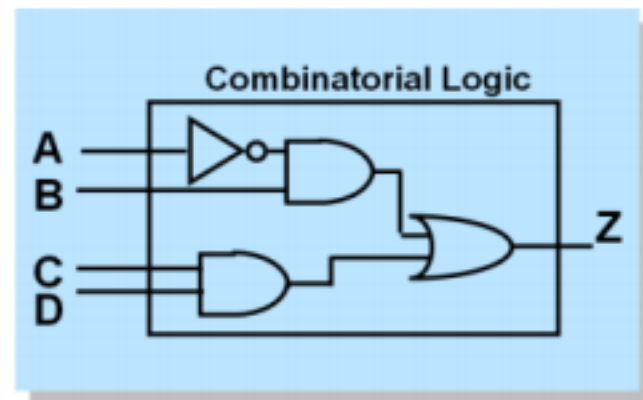
# Lookup Table (LUT)

- \* Fundamental to FPGA's
  - \* Small Static RAM (SRAM) cell
  - \* Can implement ANY logic function



A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

# Lookup Table

- \* LUT sizes vary
  - \* Xilinx Series 7 - LUT-6
  - \* Others generally LUT-4
- \* Complicates vendor comparisons
  - \* Apples v Oranges



# Synthesised Design

13	12	11	10	0
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0

13	12	11	10	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

# Testbenches

- \* Verilog code
  - \* Simulation code style
- \* 1 to 1 with module
  - \* logic.v
  - \* logic\_tb.v



# New Syntax

- \* Arrays
- \* Concatenation
- \* Symbolic values
- \* System functions and tasks
  - \* `$display`, `$time`
- \* Delays - `#1`, `#9`

# Verilog Headers

- \* C preprocessor equivalent
- \* .vh suffix
- \* Include globally

```
// logic
`define ALUFN_AND      2'b00
`define ALUFN_OR       2'b01
`define ALUFN_XOR      2'b10
`define ALUFN_PASSB    2'b11
```



# Using Headers

\* Compiler performs 'cut & paste'

```
`timescale 1 ns / 1 ps
`include "defines.vh"

...

case (fn)
  `ALUFN_AND:    sum = ...;
  `ALUFN_OR:     sum = ...;
  `ALUFN_XOR:    sum = ...;
default:        sum = ...;
endcase
```


# Delays

- \* Simulation code only
- \* `#N` - N cycle delay
- \* Units taken from module
  - \* ``timescale 1 ns / 100 ps`
- \* `#1.2` = 1.2 ns delay


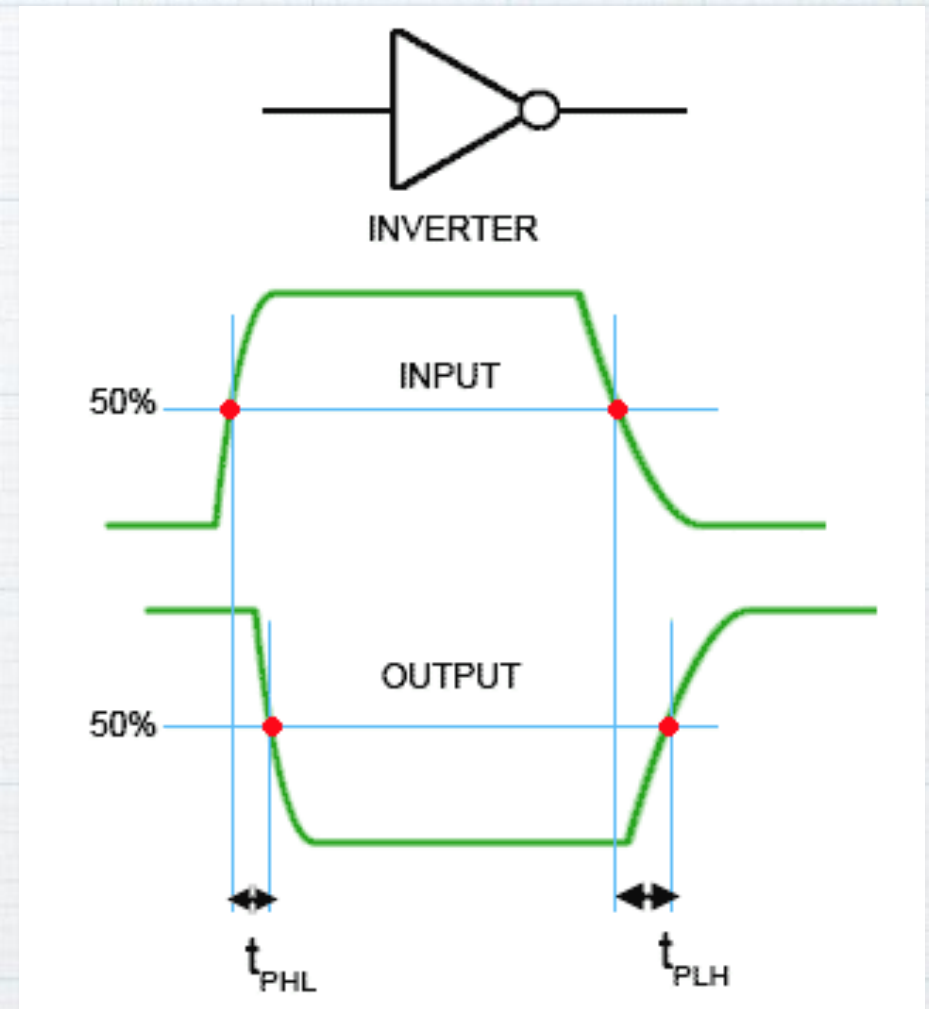
# Propagation Delay

- \* All circuitry has delays
- \* LUT's
- \* Signal routing (wires)



# Simulation Types

- \* Behavioural
  - \* 'Perfect world', no propagation delays
- \* Post-Synthesis Timing
  - \* Nominal delays
- \* Post-Implementation Timing
  - \* Most accurate, logic and signal path delays



# Lab 04 - Symbolic Values

- \* Replace binary literals
- \* Use symbolic names

# Newb Erros #1

- \* Reg vs Wire
- \* VERY confusing
  - \* Try to Google answer
- \* Error messages like:
  - \* concurrent assignment to a non-net s is not permitted



```
module logic(  
    input      [1:0]    fn,  
    input      [7:0]    a,  
    input      [7:0]    b,  
    output reg  [7:0]    sum,  
    output      s, v, n, z  
);  
  
always @*  
    case (fn)  
        default: sum = 8'b0;  
    endcase  
  
// Flag logic, leave this bit alone  
assign s = sum[7];  
assign v = 1'b0;  
assign n = sum[7];  
assign z = ~| sum;  
  
endmodule
```



# Newb Erros #2

- \* Procedural 'weirdness'
  - \* if / case statements do strange things
  - \* Inputs change, outputs do not
- \* Inferred latches
  - \* Incorrect sensitivity list
  - \* Verilog 1995 and older is prone



```
// Verilog 2001 - always combinational
// Compiler auto calculates sensitivity list
always @*
    case (fn)
        `ALUFN_AND:    sum = a & b;
        `ALUFN_OR:     sum = a | b;
        `ALUFN_XOR:    sum = a ^ b;
        default:       sum = b;
    endcase
```

```
// Verilog 2001 - maybe combinational (depends)
// Manual sensitivity list
always @(fn, a, b)
```

```
// Verilog 1995 - maybe combinational (depends)
// Manual sensitivity list
always @(fn or a or b)
```

```
// Verilog 1995 - sequential
// Manual sensitivity list
always @(posedge clock, negedge reset)
```



```
// Error!  
// sum value only changes when fn value changes  
  
always @(fn)  
    case (fn)  
        `ALUFN_AND:    sum = a & b;  
        `ALUFN_OR:     sum = a | b;  
        `ALUFN_XOR:    sum = a ^ b;  
        default:        sum = b;  
    endcase
```

```
// For combinational Verilog 2001
```


```
always @*
```



# Lab 05 - Common Errors

- \* Make deliberate errors
- \* Observe Vivado behaviour

# Stage 1 Roadmap

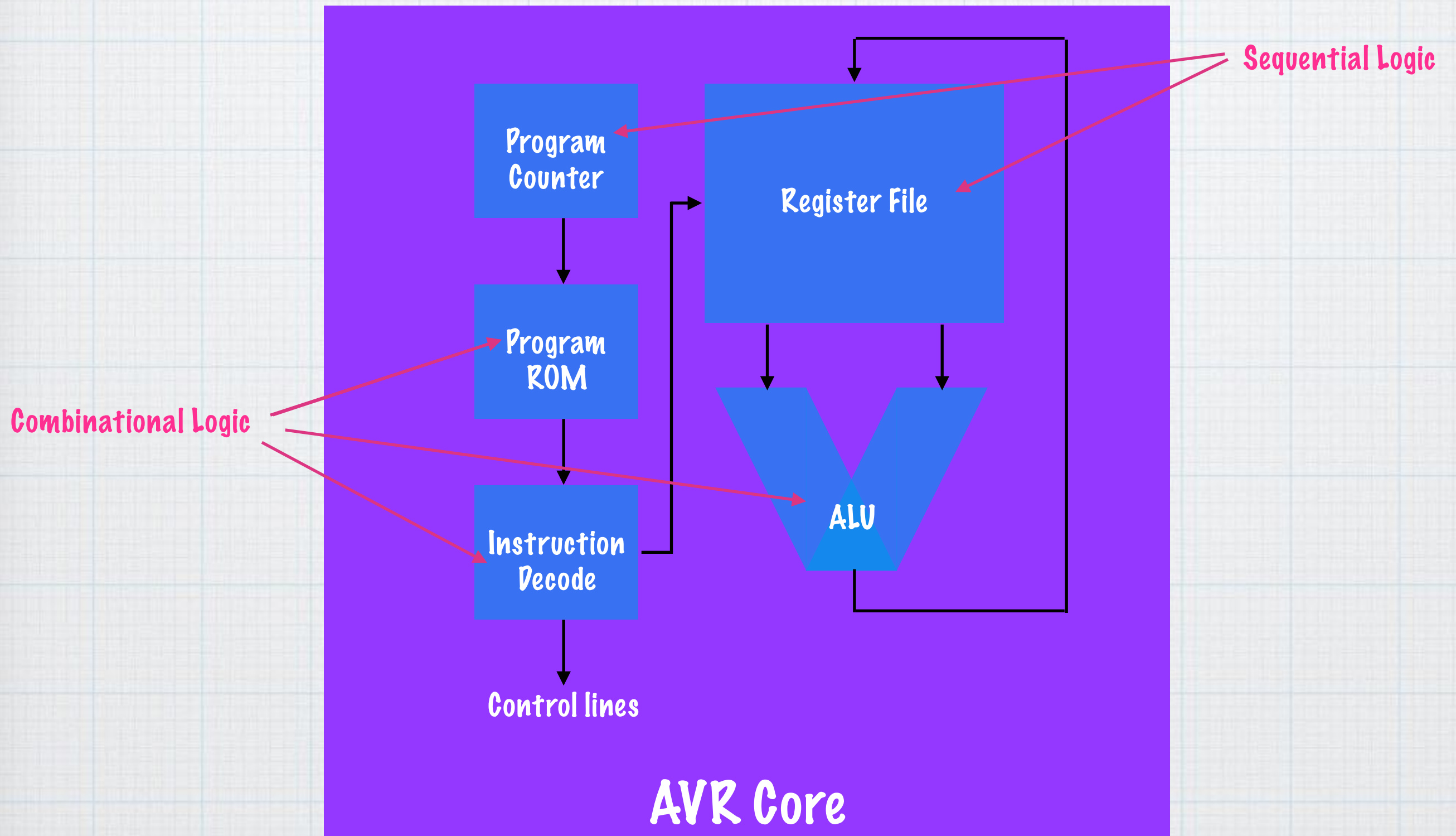



# Program ROM

```
module prog1(  
    input      [3:0]    a,      // address  
    output reg [15:0]    dout    // instruction  
);  
  
always @*  
    case (a)  
        4'h0:    dout = 16'hea05; // ldi  
        4'h1:    dout = 16'he01f; // ldi  
        4'h2:    dout = 16'h2301; // and  
        default: dout = 16'h0000; // nop  
    endcase  
  
endmodule
```

